

1. (5 points)

Consider a NPN transistor which exhibits a $v_{BE1}=0.727011$ V at $i_{C1}=1$ mA and $v_{BE2}=0.786537$ V at $i_{C2}=10$ mA. Calculate the transistor's temperature and I_s .

Boltzmann's constant = $1.38064852 \times 10^{-23}$

Charge of electron = $1.6021766208 \times 10^{-19}$

Note: In this problem, you may only submit numerical answers accurate to 0.02% or better. (i.e. If 4 is the correct answer, 3.9999 will be marked as correct, but 2+2 will be marked as incorrect.)

(a) T : ____ K

(b) I_s : ____ 10^{-18} A

Correct Answers:


- 300
- 612

2. (5 points)

In the circuit below $R_B=100k\Omega$, $R_C=1k\Omega$, $V_{CC}=10$ V, $\beta=100$, $V_{BE}=0.7$ V, and $V_{CE(sat)}=0.2$ V.

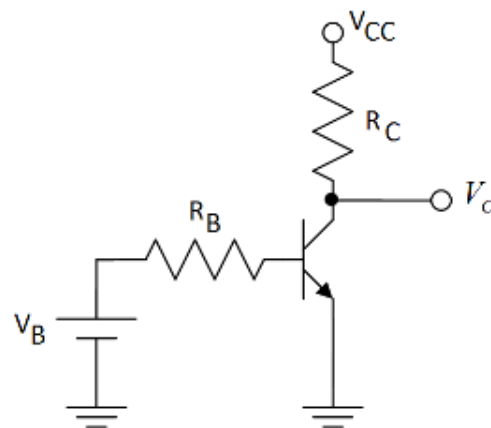- a. Calculate V_C if $V_B=0.5$ V.
- b. Calculate V_C if $V_B=2.9$ V.
- c. Calculate V_C if $V_B=14.1$ V.

Note: In this problem, you may only submit numerical answers accurate to 0.02% or better. (i.e. If 4 is the correct answer, 3.9999 will be marked as correct, but 2+2 will be marked as incorrect.)



(a) V_C : ____ V

(b) V_C : ____ V

(c) V_C : ____ V

Correct Answers:


- 10
- 7.8
- 0.2

3. (10 points)

In the circuit below $R_B=109k\Omega$, $R_C=0.12k\Omega$, $R_E=1.1k\Omega$, $V_{CC}=12$ V, $V_{EE}=-12$ V, $\beta=100$, $V_{BE}=0.7$ V, and $V_{CE(sat)}=0.2$ V.

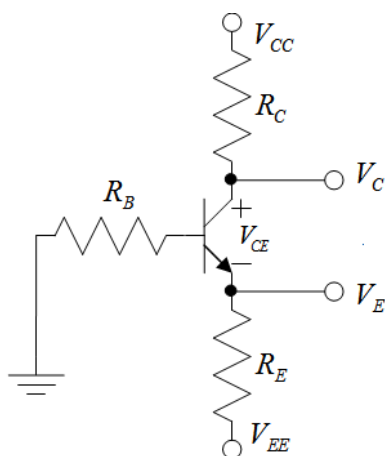- a. Calculate I_B in μ A.
- b. Calculate I_C in mA.
- c. Calculate I_E in mA.
- d. Calculate V_{CE} in V.

Note: In this problem, you may only submit numerical answers accurate to 0.02% or better. (i.e. If 4 is the correct answer, 3.9999 will be marked as correct, but 2+2 will be marked as incorrect.)



- (a) I_B : ____ μA
 (b) I_C : ____ mA
 (c) I_E : ____ mA
 (d) V_{CE} : ____ V

Correct Answers:


- 51.3403
- 5.13403
- 5.18537
- 17.68

4. (10 points)

The zener diode in the circuit below is a 1N4740A with $V_Z=10V$ @ $I_{ZT}=25mA$, $r_Z=7\Omega$. For the transistor $\beta=60$, $V_{EB}=0.7V$, and $V_{CE(sat)}=0.2V$. $V_i=-15.2V$, $R_{BZ}=186\Omega$, and $R_L=44\Omega$.

- Calculate V_o in V using the constant voltage drop model to represent the zener.
- Calculate the base current I_B in mA using the constant voltage drop model to represent the zener.
- Calculate V_o in V using the incremental model $V_{Z0} + r_Z$ to represent the zener.
- Calculate the base current I_B in mA using the incremental model $V_{Z0} + r_Z$ to represent the zener.

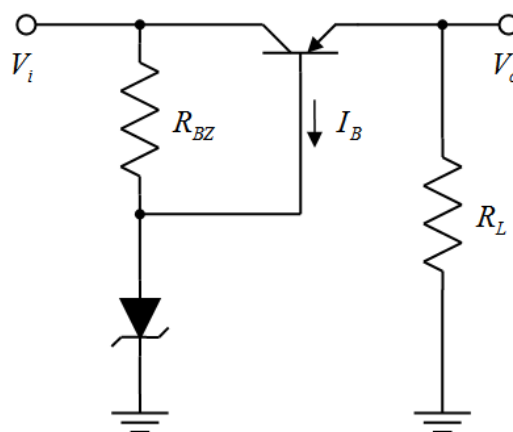Note: In this problem, you may only submit numerical answers accurate to 0.02% or better. (i.e. If 4 is the correct answer, 3.9999 will be marked as correct, but 2+2 will be marked as incorrect.)



- (a) V_o : ____ V
 (b) I_B : ____ mA
 (c) V_o : ____ V
 (d) I_B : ____ mA

Correct Answers:


- -9.3
- 3.46498
- -9.29658
- 3.4637

5. (10 points)

For the transistor in the circuit below $\beta=100$, $V_{BE}=0.7V$, and $V_{CE(sat)}=0.2V$. $V_{CC}=14V$, $R_1=1028\Omega$, $R_2=2036\Omega$, and $R_E=42\Omega$.

- Calculate the base current I_B in mA .
- Calculate V_E in V .

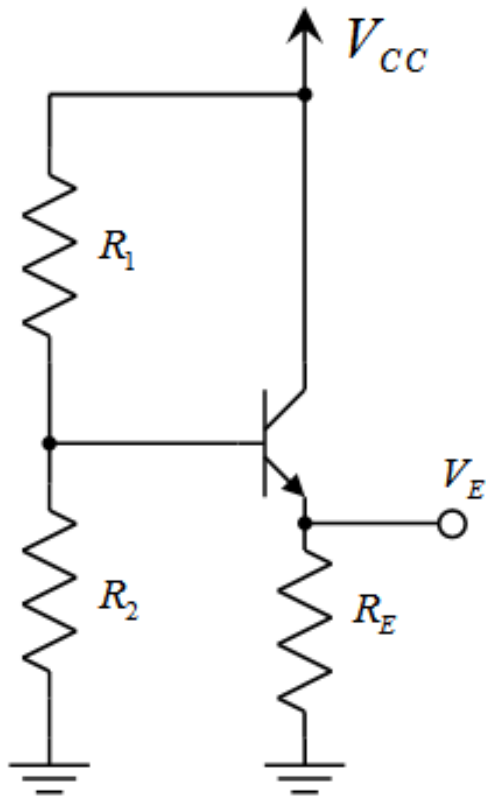Note: In this problem, you may only submit numerical answers accurate to 0.02% or better. (i.e. If 4 is the correct answer, 3.9999 will be marked as correct, but 2+2 will be marked as incorrect.)



(a) I_B : ____ mA

(b) V_E : ____ V

Correct Answers:


- 1.74674
- 7.40968

6. (10 points)

For the transistors in the circuit below $\beta=100$, $V_{BE}=0.7V$, and $V_{CE(sat)}=0.2V$. $V_{CC}=15V$, $R_1=0.96M\Omega$, $R_2=1.44M\Omega$, and $R_C=10\Omega$.

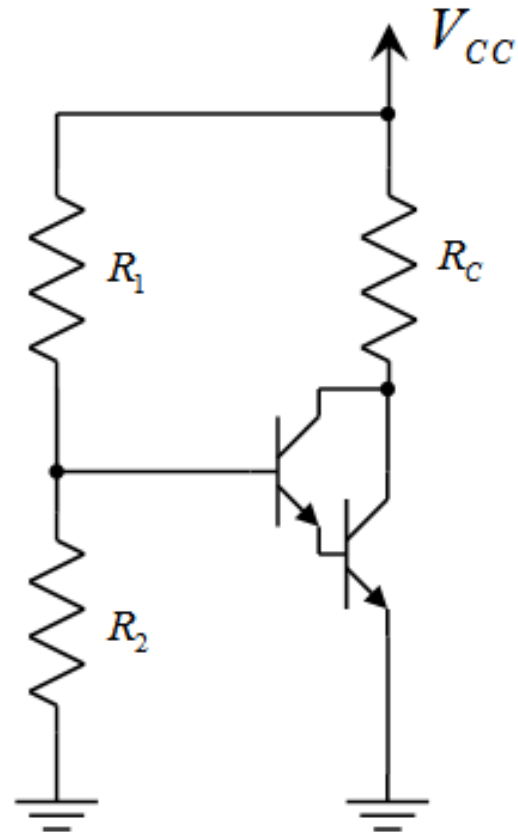- a. Calculate the base current I_B in μA .
- b. Calculate the collector current I_C in mA .
- c. Calculate the emitter current I_E in mA .

Note: In this problem, you may only submit numerical answers accurate to 0.02% or better. (i.e. If 4 is the correct answer, 3.9999 will be marked as correct, but 2+2 will be marked as incorrect.)




(a) I_B : ____ μA

(b) I_C : ____ mA

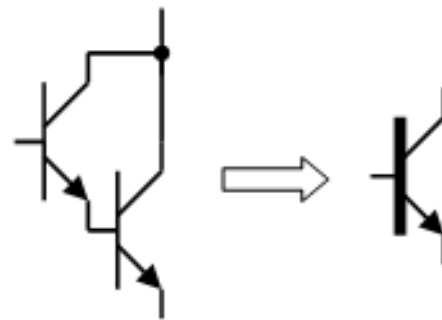(c) I_E : ____ mA

When a couple of transistors are arranged in the manner shown in the figure above, the resulting combination is called a Darlington Pair, which is often represented with the symbol in the figure below. Calculate $\beta_{Darlington}$ of the equivalent transistor.



(d) $\beta_{Darlington}$: —

Correct Answers:


- 13.1944
- 134.583
- 134.597
- 10200

7. (10 points)

For the transistor in the amplifier below $\beta=100$, $V_{BE}=0.7V$, and $V_{CE(sat)}=0.2V$. Also $R_S=50\Omega$, $R_L=142\Omega$, $V_{CC}=13.6V$, $R_1=6946\Omega$, $R_2=3643\Omega$, $R_C=906\Omega$, and $R_E=501\Omega$. Assume $V_T=0.025V$.

- Calculate g_m in $\frac{A}{V}$.
- Calculate r_π in Ω .
- Calculate the voltage gain A_V in $\frac{V}{V}$.

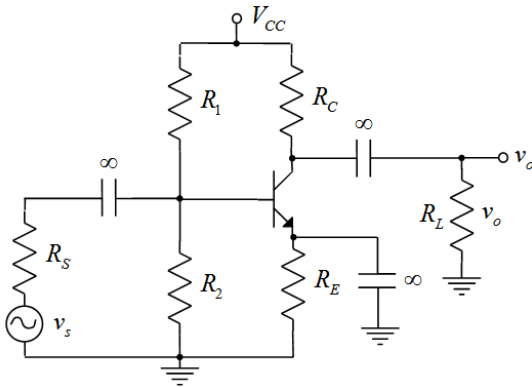Note: In this problem, you may only submit numerical answers accurate to 0.02% or better. (i.e. If 4 is the correct answer, 3.9999 will be marked as correct, but 2+2 will be marked as incorrect.)



- g_m : — $\frac{A}{V}$
- r_π : — Ω
- A_V : — $\frac{V}{V}$

Correct Answers:


- 0.300347
- 332.949
- -31.4837

8. (10 points)

For the transistor in the amplifier below $\beta=100$, $V_{EB}=0.7V$, $V_A=97V$, and $V_{EC(sat)}=0.2V$. Also $R_S=50\Omega$, $R_L=2100\Omega$, $I_E=8.585mA$, $R_B=94.117\text{ k}\Omega$, $R_C=588\Omega$. Assume $V_T=0.025V$.

- Calculate g_m in $\frac{A}{V}$.
- Calculate r_π in Ω .
- Calculate the voltage gain A_V in $\frac{V}{V}$.

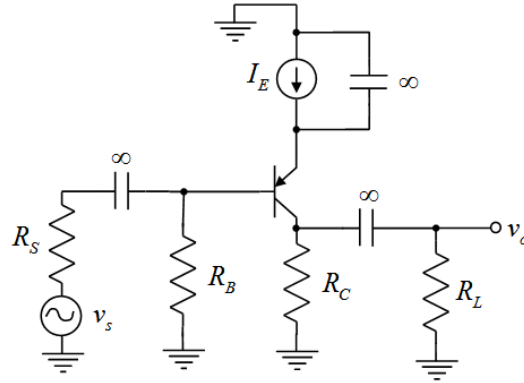Note: In this problem, you may only submit numerical answers accurate to 0.02% or better. (i.e. If 4 is the correct answer, 3.9999 will be marked as correct, but 2+2 will be marked as incorrect.)



- g_m : — $\frac{A}{V}$
- r_π : — Ω
- A_V : — $\frac{V}{V}$

Correct Answers:


- 0.34
- 294.118
- -128.27

9. (10 points)

For both transistors in the amplifier below $\beta=100$, $V_{EB}=0.7V$, $V_A=98V$, and $V_{EC(sat)}=0.2V$. The zener diode can be modeled as a constant voltage source of $V_Z=3.3V$. Also $R_S=50\Omega$, $R_L=2710\Omega$, $R_B=93.535\text{ k}\Omega$, $R_C=584\Omega$, $R_1=298\Omega$, and $R_2=580\Omega$. Assume $V_T=0.025V$ and $V_{DC}=15V$.

- Calculate g_m in $\frac{A}{V}$.
- Calculate r_π in Ω .
- Calculate the voltage gain A_V in $\frac{V}{V}$.

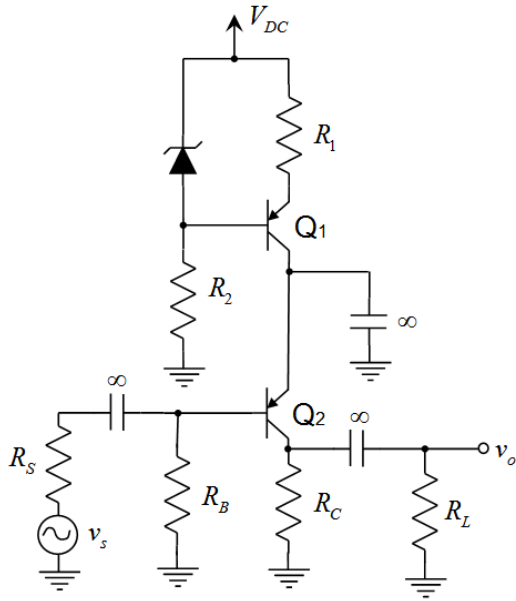Note: In this problem, you may only submit numerical answers accurate to 0.02% or better. (i.e. If 4 is the correct answer, 3.9999 will be marked as correct, but 2+2 will be marked as incorrect.)



(a) $g_m : \text{---} \frac{A}{V}$

(b) $r_\pi : \text{---} \Omega$

(c) $A_v : \text{---} \frac{V}{V}$

Correct Answers:


- 0.342117
- 292.298
- -134.653

10. (10 points)

For the transistor in the common base amplifier below $\beta=100$, $V_{BE}=0.7V$, and $V_{CE(sat)}=0.2V$. Also $I_E=9.4mA$, $R_S=50\Omega$, $R_L=1260\Omega$, $R_C=620\Omega$, $V_T=0.025V$, $V_{CC}=15V$, and $V_{EE}=-15V$.

- Calculate $A_v = \frac{v_o}{v_s}$ in $\frac{V}{V}$.
- Calculate R_i in Ω .
- Calculate R_o in Ω .

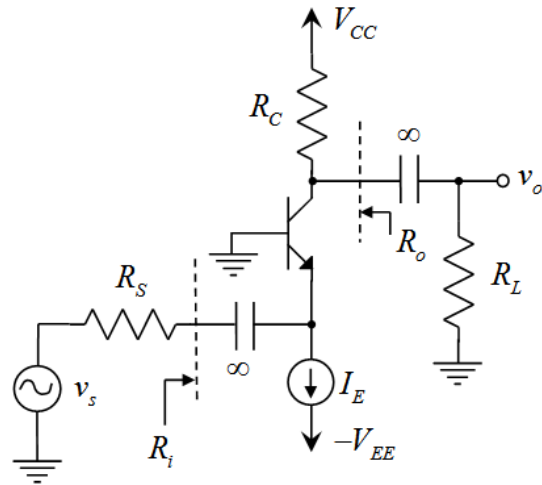Note: In this problem, you may only submit numerical answers accurate to 0.02% or better. (i.e. If 4 is the correct answer, 3.9999 will be marked as correct, but 2+2 will be marked as incorrect.)



(a) $A_v : \text{---} \frac{V}{V}$

(b) $R_i : \text{---} \Omega$

(c) $R_o : \text{---} \Omega$

Correct Answers:


- 7.81278
- 2.65957
- 620

11. (5 points)

The circuit below is used to control a DC motor using a micro-controller for which logic one is 3V and logic zero is 0V. The motor consumes a maximum of 0.48A when turned on. For both Q_1 and Q_2 : $\beta=100$, $V_{BE}=V_{EB}=0.7V$, and $V_{CE(sat)}=V_{EC(sat)}=0.2V$. Also $R_C=11.2k\Omega$ and $V_{DC}=11.8V$.

- Calculate the maximum allowed value of R_{B1} in Ω .
- Calculate the maximum allowed value of R_{B2} in Ω .

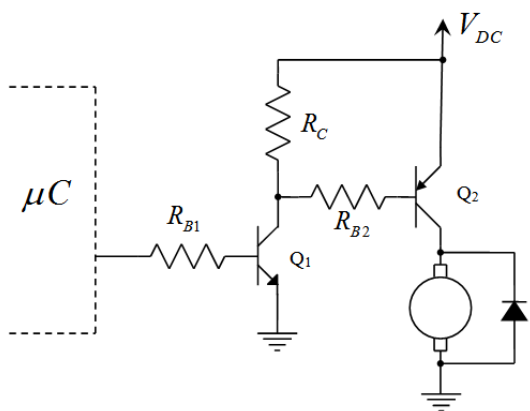Note: In this problem, you may only submit numerical answers accurate to 0.02% or better. (i.e. If 4 is the correct answer, 3.9999 will be marked as correct, but 2+2 will be marked as incorrect.)



(a) R_{B1} : ____ Ω

(b) R_{B2} : ____ Ω

Correct Answers:

- 39412.5
- 2270.83


12. (5 points)

The circuit below is a Diode-Transistor-Logic (DTL) NAND gate for which logic one is a voltage greater or equal than 1.4V and logic zero is a voltage less or equal than 0.2V. For the transistor $\beta=100$, $V_{BE}=0.7V$, and $V_{CE(sat)}=0.2V$. All the diodes can be represented as a constant voltage drop of $V_D=0.7V$; also $R_C=1360\Omega$, $R_{B1}=1350\Omega$, $R_{B2}=6750\Omega$, and $V_{DC}=5V$. Both V_a and V_b can only be 0V (logic zero) or 5V (logic one).

- a. Calculate the base current I_B in mA when the output V_o is logic zero.

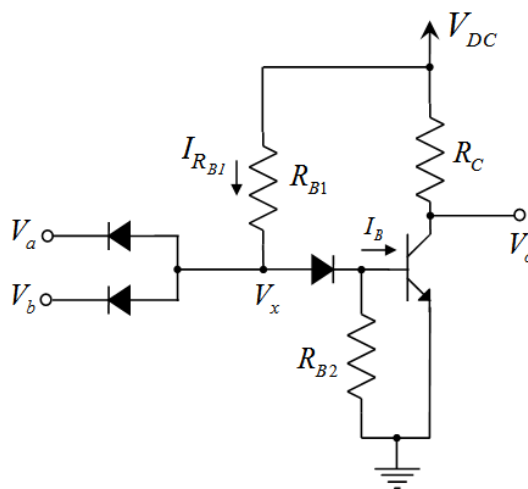- b. Calculate the current through R_{B1} ($I_{R_{B1}}$) in mA when the output V_o is logic one.

Note: In this problem, you may only submit numerical answers accurate to 0.02% or better. (i.e. If 4 is the correct answer, 3.9999 will be marked as correct, but 2+2 will be marked as incorrect.)



(a) I_B : ____ mA

(b) $I_{R_{B1}}$: ____ mA

Correct Answers:

- 2.56296
- 3.18519