


1. (12 points)

(a) In the figure,  $R = 17 \Omega$ . Find,  $V_{th}$  and  $R_{th}$ , for the Thevenin equivalent seen by the  $9 \Omega$  resistor at the bottom, as per the figure below the circuit.

$$V_{th} = \text{---} V$$

$$R_{th} = \text{---} \Omega$$

Figure:

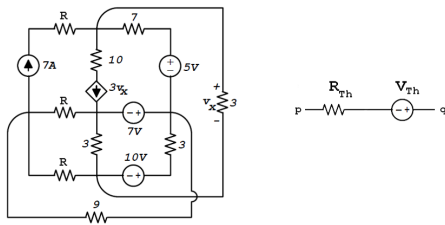

(b) Replace the  $9 \Omega$  resistor for a resistance that will drain maximum power off the circuit. What is the value of that resistance,  $R_X$  in ohms, and of that  $P_{MAX}$  in watts.

$$R_X = \text{---} \Omega$$

$$P_{MAX} = \text{---} W$$


Correct Answers:

- 69.0814
- 8.85222
- 8.85222
- 134.775

2. (12 points)

What is  $V_{th}$  and  $R_{th}$  'seen' by  $R_x$  when  $I_s = 20 A$ ,  $R = 17 \Omega$  and  $R_x = 5 \Omega$ . Determine this, by simple observation, do not use calculator, nor pen or paper.

Figure:

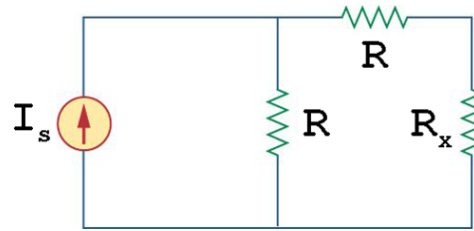

$$V_{th} = \text{---} V$$

$$R_{th} = \text{---} \Omega$$


Correct Answers:

- 340
- 34

3. (12 points)

At the port 'ab' find the  $V_{oc}$ , in volts, the open circuit voltage; and also find  $I_{sc}$ , the shortcircuit current, in amps. And determine  $V_{TH}$  and  $R_{TH}$  for its Thevenin equivalent circuit, as per the figure below.  $R_1$  is 27,  $R_2$  is 17,  $R_3$  is 29 all in ohms.  $V$  is 7 volts, and  $I$  is 20 amps.

Figure:

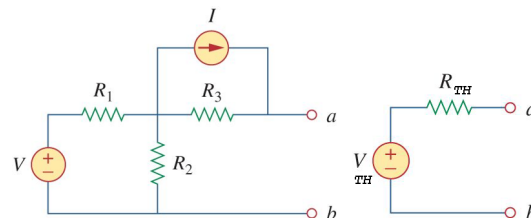

$$V_{th} = \text{---} V$$

$$R_{th} = \text{---} \Omega$$

$$V_{oc} = \text{---} V$$

$$I_{sc} = \text{---} A$$

Correct Answers:

- 582.705
- 39.4318
- 582.705
- 14.7775



$$R_{Nab} = \text{--- } \Omega$$

$$R_{Ncd} = \text{--- } \Omega$$

$$I_{ab} = \text{--- } A$$

$$I_{cd} = \text{--- } A$$


Correct Answers:

- 7.53478
- 5.3797
- -2.77966
- 6.10386

### 8. (13 points)

The resistor  $R_2 = 4.44444$  ohms is absorbing the maximum power that can be extracted out of the rest of the circuit. What is the value of the resistor  $R_1$ , in ohms, and what is the mentioned maximum power in  $R_2$ , in watts.  $R_3 = 8$  ohms,  $V_1 = 6$  volts,  $V_2 = 6$  volts.

Figure:

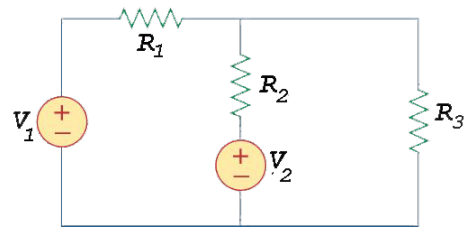

$$R_1 = \text{--- } \Omega$$

$$P_{\max} = \text{--- } W$$

Correct Answers:

- 10
- 0.625