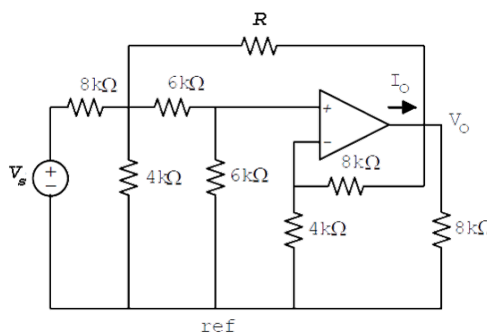


12. (12 points)

Question: In the circuit in figure below, obtain the output voltage  $V_o$ , in volts, and current  $I_o$ , in mA. This exercise attempts to erase the misconception that the output current of the op amp is zero, that is almost never true! The values  $R = 7 \text{ k}\Omega$  and  $V_s = 16 \text{ volts}$ .

Figure:



$I_o = \text{___ mA}$

$V_o = \text{___ V}$

Correct Answers:

- 1.98462
- 7.75385

13. (12 points)


For the instrumentation amplifier in the figure,  $R = 21 \text{ kilo ohms}$ ,  $R_x = 34 \text{ kilo ohms}$ ,  $V_1 = 30 \text{ millivolts}$ ,  $V_2 = 15 \text{ millivolts}$ .

(a) Compute and report  $V_o$ , in millivolts;

(b) Now assume that the op amp is powered by a source  $V_{cc} = \pm 11 \text{ volts}$ . What is the maximum input voltage difference ( $V_1 - V_2$ ) that will not saturate the op amp.

**Hint:** Work out  $V_o$  as a function of  $R_x$ ,  $R$ ,  $V_1$  and  $V_2$  first, and then substitute numerical values.

Figure:

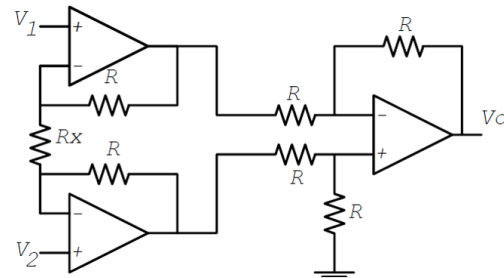

$V_o = \text{___ mV}$

$(V_1 - V_2)_{\max} = \text{___ V}$

Correct Answers:

- -33.5294
- 4.92105

14. (12 points)


In the circuit shown,  $R$  is 10 kilo-ohms. Both op amps are identical and powered from a -22/22 volts power supply. Determine:

(a) what is the output voltage of each op amps,  $V_{oa}$ ,  $V_{ob}$  and  $V_{na}$ , if we ignore the power supply; ;

(b) what is the output voltage of each op amp,  $V_{oa}$ ,  $V_{ob}$  and  $V_{na}$ , if we consider the power supply;

(c) To reduce the chance of saturation, should we increase or decrease  $R$  (enter 1 for increase, and minus 1 for decrease and 0 for no change).

Figure:

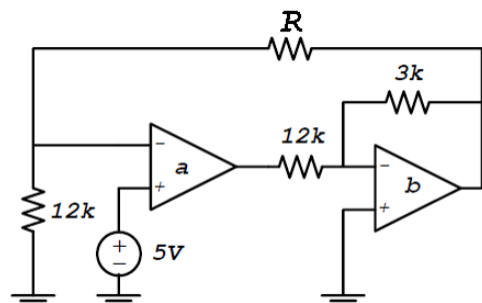

(a)  $V_{oa} = \text{___ V}$

$V_{na} = \text{___ V}$

$$V_{ob} = \_\_\_ V$$

(b)  $V_{oa} = \_\_\_ V$

$$V_{na} = \_\_\_ V$$

$$V_{ob} = \_\_\_ V$$

(c) To reduce the chance of saturation, should we increase or decrease  $R$   $\_\_\_$

Correct Answers:

- -36.6667
- 5
- 9.16667
- 22
- -3
- -5.5
- 0


15. (12 points)

In the circuit shown in the figure below, the feedback resistor  $R = 3$  kilo-ohms.

(a) What is the output voltage,  $V_o$ , in volts?;

(b) If the op amp is powered from a -16/24 V power supply, what should be the value of  $R$  to saturate the amplifier,  $R_{sat}$  in kilo-ohms?

Figure:

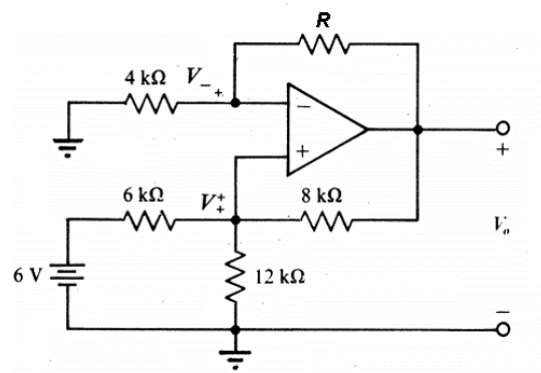

$$V_o = \_\_\_ V$$

$$R_{sat} = \_\_\_ k\Omega$$

Correct Answers:

- 11.2
- 5

16. (12 points)


In the op amp circuit shown below, the feedback resistor is  $R_f = 5$  kilo-ohms.

(a) What is the output voltage,  $V_o$ , in volts, if we ignore the limits imposed by the power supply?;

(b) If the op amp is powered from a -27/24 V power supply, what should be the minimum value of  $R_f$  that gets the amplifier into saturation,  $R_{sat}$  in kilo-ohms?

(c) Under the saturation conditions attained in part (b) above, what is the output current of the op amp,  $I_o$  in milliamps, (assume the current  $I_o$  pointing to the right)?

Figure:

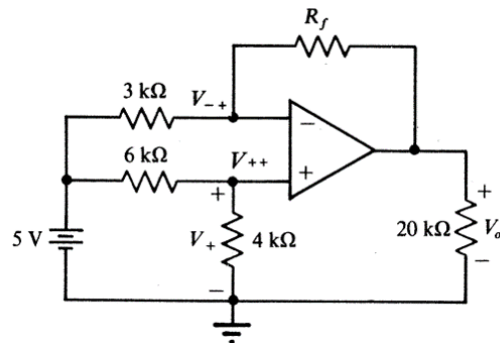

(a)  $V_o = \_\_\_ V$

(b)  $R_{sat} = \_\_\_ k\Omega$

(c)  $I_o = \_\_\_ mA$

Correct Answers:

- -3
- 29
- -2.35


17. (12 points)

In the circuit of the figure,  $R = 8 k\Omega$ .

(a) What is the output voltage,  $V_o$ , in volts?;

(b) What is the output current,  $I_o$ , in milliamps?

Figure:

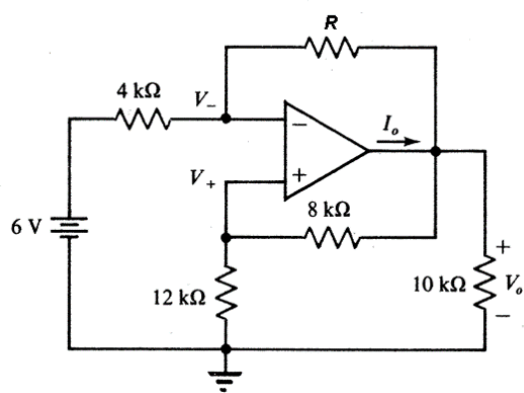

(a)  $V_o = \text{---} V$

(b)  $I_o = \text{---} mA$

*Correct Answers:*

- 15
- 3