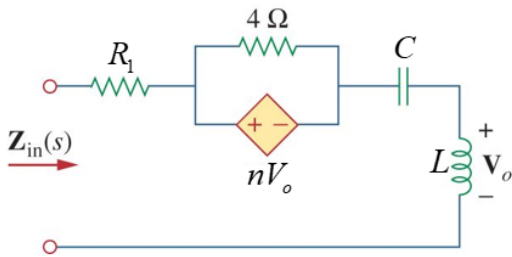


1. (17 points)

[17 marks, approx 15 mins] For the circuit in the figure below, find the input impedance,  $Z_{in}(s)$ , as a function of  $s$ , the Laplace variable. (a) Do a Bode amplitude plot and determine the frequency at which  $Z_{in}$  is minimum,  $\omega_o$ , in rad/s. On the Bode amplitude plot, determine the +3 dB frequencies, (b)  $\omega_1$  and (c)  $\omega_2$ , also in rad/s. Compute (d) the bandwidth, in rad/s; and (e) the quality factor. Then, scale the circuit so that the circuit uses 10 k $\Omega$  resistors instead, and so that the minimum impedance occurs at 20 krad/s. After scaling, what will be the values of the reactive elements, (f)  $L$  and (g)  $C$ ?. (N.B. scaling won't affect the dependent source coefficient  $n$ .) The reactive element values are  $L = 7.8$  H, and  $C = 0.6$  F. The resistor  $R_1 = 4\Omega$ . The dependent source coefficient  $n = 3.5$ .

Figure corresponding to Question 1 of this final exam.



DO NOT GUESS ANSWERS. The right answer without the correct procedure is still an invalid response.

- (a)  $\omega_o = \underline{\hspace{2cm}}$  rad/s  
 (b)  $\omega_1 = \underline{\hspace{2cm}}$  rad/s  
 (c)  $\omega_2 = \underline{\hspace{2cm}}$  rad/s  
 (d) Bandwidth =  $\underline{\hspace{2cm}}$  rad/s  
 (e) Quality factor =  $\underline{\hspace{2cm}}$  no units  
 (f)  $L_{new} = \underline{\hspace{2cm}}$  H  
 (g)  $C_{new} = \underline{\hspace{2cm}}$  F

Answer(s) submitted:

- 0.2179068
- 0.1542662
- 0.3078016

- 0.153535
- 1.419262
- 0.2124591
- 0.000000002614882

(correct)

2. (9 points)


[9 marks, approx 7 minutes.] A transfer function  $H(s)$  is approximated by the Bode amplitude plot in the figure below. Observe that there is a damping factor associated with the frequency 'd' in the figure. A student concludes that the transfer function can be written as

$$H(s) = \frac{ks(s+b)^2}{(s+a)(s+c)^2(s^2+ms+n)}$$

If you agree with the student, compute and report the constant 'k' on the numerator. If you don't agree with the student, write the correct transfer function on your procedure-page (that you will scan and upload as a PDF), and compute and report below in the entry box the value of the correct 'k' (the one for your transfer function). The values for your question are:  $a = 900$ ,  $b = 1550$ ,  $c = 2800$ ,  $d = 12000$ ,  $m = 2400$ ,  $n = 1.44 \times 10^8$ . All in rad/s except the last two. The decibels level at the highest plateau is  $A_x = -176.596$  dB.

N.B. If you are entering results in scientific notation, example  $1.234 \times 10^{-3}$ , use an uppercase E to enter 1.234E-3, never type 1.234e-3.

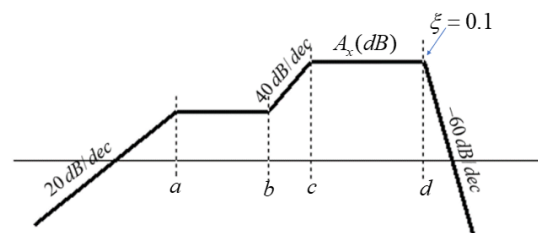Bode amplitude plot of a transfer function  $H(s)$



The right value for the constant k =  $\underline{\hspace{2cm}}$

Answer(s) submitted:

- 0.001596992416


(incorrect)

3. (8 points)

[8 marks, approx 5 mins] Select the values of the capacitors for the bandpass filter in the top right part of the figure, so that its Bode amplitude plot (frequency response) corresponds to the

dB-versus-rad/s-plot on the lower left corner of the figure below. All op amps are ideal.  $R_1 = R_2 = R_3 = 13 \text{ k}\Omega$  (that is, all those three resistors have the same value.) Also, if the bandpass gain is to be (the decibels on the plateau)  $A_{dB} = 14 \text{ dB}$ , what should be the value of the feedback resistor  $R_f$  in kilo ohms? For your question,  $\omega_L = 320 \text{ rad/s}$  and  $\omega_H = 16000 \text{ rad/s}$ .
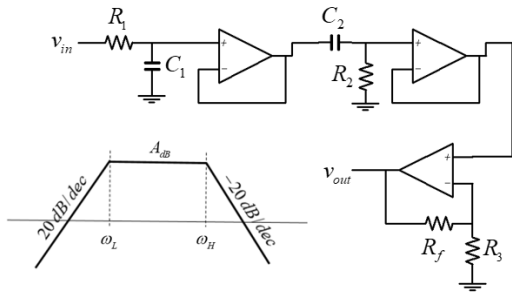
#### An active bandpass filter and its Bode frequency response



$$C_1 = \text{___ nF}$$

$$C_2 = \text{___ nF}$$

$$R_f = \text{___ k}\Omega$$

Answer(s) submitted:


- 4.807692
- 240.3846
- 52.1543403175

(correct)
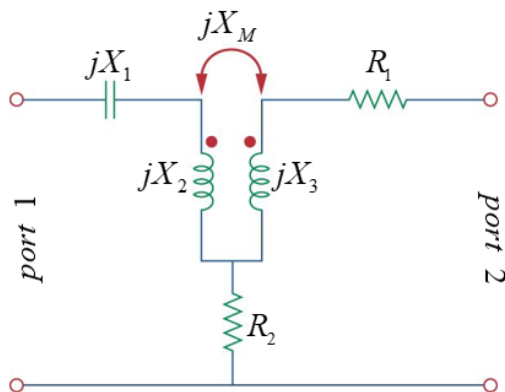
#### 4. (16 points)

[16 marks, approx. 15 mins.] For the two-port network in the figure below, compute and report the hybrid parameters. For your question,  $X_1 = -5 \Omega$ ,  $X_2 = 3 \Omega$ ,  $X_3 = 8 \Omega$ ,  $X_M = 6 \Omega$ ,  $R_1 = 2 \Omega$ ,  $R_2 = 16 \Omega$ .

Two port network to find the hybrid parameters.



$$h_{11} = \text{___} + j \text{___}$$

$$h_{12} = \text{___} + j \text{___}$$

$$h_{21} = \text{___} + j \text{___}$$

$$h_{22} = \text{___} + j \text{___}$$

Answer(s) submitted:

- 0.04639175
- -0.02061855
- -0.783505154639
- -3.7731958
- 0.237113402062

(score 0.25)


#### 5. (20 points)

A balanced three-phase system has a distribution wire with impedance  $Z_1 = 10.5 + j14 \Omega$  per phase. The system supplies two three-phase loads that are connected in parallel. The first is a balanced wye-connected load that absorbs a total  $S_a = 350 \text{ kVA}$  apparent power at a power factor  $pf = 0.8$  lagging. The second load is a balanced delta-connected load with impedance of  $Z_\Delta = 21 + j16.8 \Omega$  per phase. The magnitude of the line voltage at the loads is  $V_{line}^{load} = 2400 V_{rms}$ . Find:

(a) Magnitude of the line voltage at the source: \_\_\_  $V_{rms}$

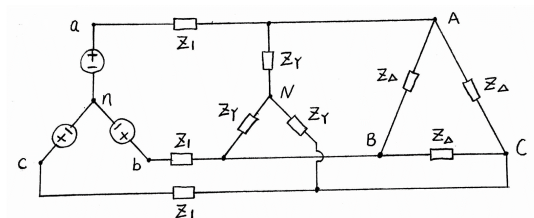(b) Total complex power of the two loads: \_\_\_ + j \_\_\_  $\text{kVA}$

Three phase balanced system with two loads in parallel.



Answer(s) submitted:

- 9636.48998611
- 781.74216
- 611.39372

(score 0.666667)

#### 6. (15 points)


The circuit below contains two ideal transformers, where  $V_s = 35 \angle 0^\circ \text{ V}$ ,  $R_1 = 6 \Omega$ ,  $R_2 = 5 \Omega$ ,  $R_3 = 7 \Omega$ ,  $Z_{c1} = -j6 \Omega$ ,  $Z_{c2} = -j5 \Omega$ , and  $Z_L = j8 \Omega$ . The turns ratios are  $n_1 = 0.5$ , and  $n_2 = 2$ .

Find:

(a) Current  $I$  at the source: \_\_\_\_ A with a phase: \_\_\_\_ deg.

(b) Voltage  $V_o$ : \_\_\_\_ V with a phase: \_\_\_\_ deg.

**Circuit with two ideal transformers.**

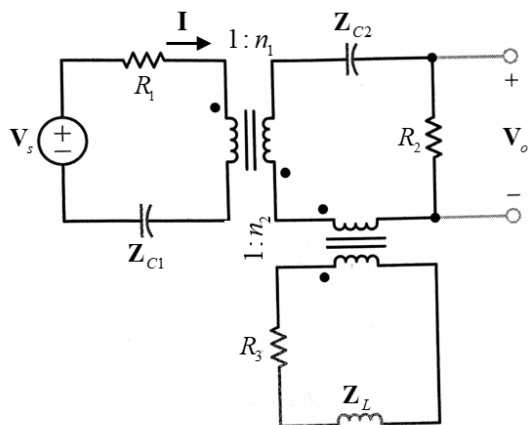

Answer(s) submitted:


- 0.2039577
- -36.469234
- 2.039577170
- 143.53076561

(correct)

7. (15 points)

In the second-order circuit below,  $V_1 = 12V$ ,  $V_2 = 24V$ ,  $R_1 = 15\Omega$ ,  $R_2 = 7\Omega$ ,  $L = 1.1H$ , and  $C = 0.02F$ . Find the answers in (a) through (e) below:

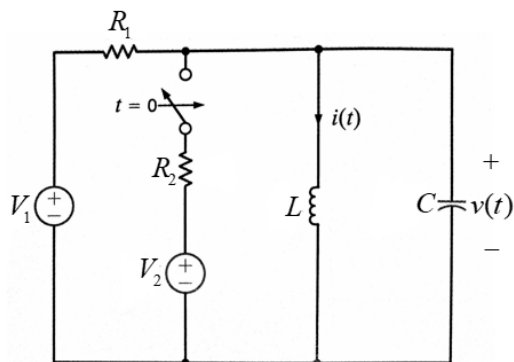**Second Order Circuit where the switch closes at  $t = 0$ .**



(a)  $v(0^+) =$  \_\_\_\_ V.

(b)  $i(0^+) =$  \_\_\_\_ A.

(c)  $\frac{dv}{dt}(0^+) =$  \_\_\_\_ V/s.

(d)  $\frac{di}{dt}(0^+) =$  \_\_\_\_ A/s.

(e)  $v(\infty) =$  \_\_\_\_ V.

(f)  $i(\infty) =$  \_\_\_\_ A.

Answer(s) submitted:

- 0
- 4/5
- 171.428571
- 0
- 0
- 4.228571

(correct)